


## CSE 234 Logic Circuits and Digital Design

### Lab 6 – FSM with Datapath

 **Lab Session (Exact Duration: 90min):**

C code:

```
while(goi==0);
x = xi;
y = yi;
z = 0;
diff = x - y;
diff2 = diff;
while(diff > 0)
{
    if (diff>10)
    {
        z = z + diff2;
    }
    else
    {
        z = z + 5;
    }
    diff = diff - 1;
}
```



- First draw high-level state machine.
- Design datapath on Logisim.
- Design your FSM controller using Logisim and combine datapath and controller in Logisim.
- Simulate your resultant circuit to be sure it works flawless.

**Rules:**

DO NOT USE ANALYZE CIRCUIT PROPERTY OF LOGISIM. You can use multiplier subtractor or adder in Logisim. Using less components makes a better score. X, y, z, diff and diff2 are registers in datapath. Assume 8 bit numbers.

**Demo Session:**

During demo, explain and simulate each step of your design. Do not forget you only have at most 4 minutes for that. Also you will answer any questions asked by the TA.